

main ▾

1 Branch

0 Tags

Go to file

Go to file

Code

⋮

This branch is [1 commit ahead of naavaneetha/D-FLIPDLOP-NEGEDGE:main](#) .

**23008859** Update README.md 2 minutes ago

db	EXP8	3 months ago
incremental_db	EXP8	3 months ago
output_files	EXP8	3 months ago
simulation	EXP8	3 months ago
DFLIPFLOPNEGEDGE.qpf	EXP8	3 months ago
DFLIPFLOPNEGEDGE.qsf	EXP8	3 months ago
DFLIPFLOPNEGEDGE.qws	EXP8	3 months ago
DFLIPFLOPNEGEDGE.v	EXP8	3 months ago
DFLIPFLOPNEGEDGE.v.bak	EXP8	3 months ago
LICENSE	Initial commit	3 months ago
README.md	Update README.md	2 minutes ago
Waveform1.vwf	EXP8	3 months ago

**README**

License

# D-FLIPDLOP-NEGEDGE

**AIM:**

To implement D flipflop using verilog and validating their functionality using their functional tables


**SOFTWARE REQUIRED:**

Quartus prime

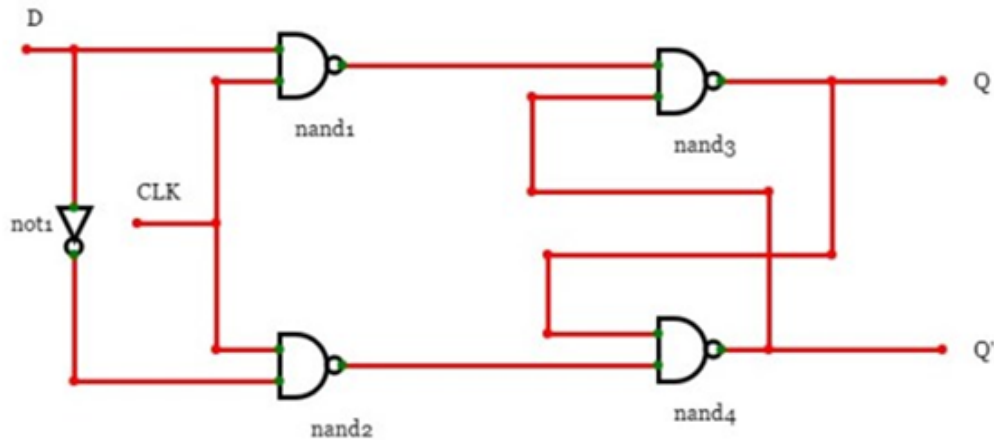**THEORY**

D Flip-Flop

D flip-flop operates with only positive clock transitions or negative clock transitions. Whereas, D latch operates with enable signal. That means, the output of D flip-flop is insensitive to the changes in the input, D except for active transition of the clock signal. The circuit diagram of D flip-flop is shown in the following figure.



This circuit has single input D and two outputs  $Q_t$  &  $Q_t'$ . The operation of D flip-flop is similar to D Latch. But, this flip-flop affects the outputs only when positive transition of the clock signal is applied instead of active enable. The following table shows the state table of D flip-flop.

D	$Q_{t+1}$
0	0
1	1

Therefore, D flip-flop always Hold the information, which is available on data input, D of earlier positive transition of clock signal. From the above state table, we can directly write the next state equation as  $Q_{t+1} = D$

D	$Q_{t+1}$
0	$Q_t$
1	$Q_t'$

Next state of D flip-flop is always equal to data input, D for every positive transition of the clock

signal. Hence, D flip-flops can be used in registers, shift registers and some of the counters.

### Procedure

- 1.Type the program in Quartus software.
- 2.Compile and run the program.
- 3.Generate the RTL schematic and save the logic diagram.
- 4.Create nodes for inputs and outputs to generate the timing diagram.
- 5.For different input combinations generate the timing diagram.


### PROGRAM

/\* Program for flipflops and verify its truth table in quartus using Verilog programming. Developed by: ROSHINI S RegisterNumber: 212223230174


```
module DFLIPFLOPNEGEDGE(D,Clock,reset,Q);  
input D,reset,Clock;  
output reg Q;  
always @ (negedge Clock)  
if(!reset)  
Q <= 0;  
else  
Q <= D;  
endmodule
```



### RTL LOGIC FOR FLIPFLOPS

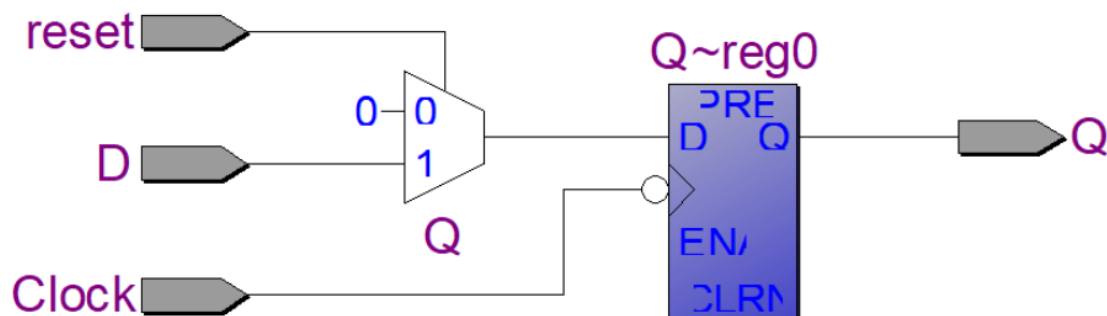

## TIMING DIGRAMS FOR FLIP FLOPS

 

## RESULTS

Thus the program to implement a D flipflop using verilog and validating their functionality using their functional tables.

## Releases

No releases published

## Packages

No packages published

## Languages

- VHDL 49.0%
- Stata 21.0%
- HTML 18.7%
- Verilog 9.6%
- Standard ML 1.7%